



# The Evolution of the Digital Revolution: Basic Theory

An Online Continuing Education Course for Engineers

**Course Number: IC-3010**

**Credit: 3 Hours / 3 PDH / 3 CPD**

# **The Evolution of the Digital Revolution Basic Theory**

**Copyright © February 2010**

# Table of Contents

| Subject                                 | Page #'s |
|---|----------|
| 1. Introduction                         | 4        |
| 2. The Binary Number System             | 4 - 5    |
| 3. The Hexadecimal System               | 5 - 6    |
| 4. Binary Coded Decimal System          | 6        |
| 5. AND, OR, and NOT Logical Functions   | 7 - 9    |
| 6. NOR's and NANDS                      | 9 - 10   |
| 7. Exclusive OR (XOR)                   | 10 - 11  |
| 8. Multiplexors and De Multiplexors     | 11-13    |
| 9. Boolean Algebra                      | 14-15    |
| 10. Half Adder                          | 15       |
| 11. Full Adder                          | 15-17    |
| 12. Digital Computer Memory             | 17-22    |
| 13. Computer Clocks or Timing Circuits  | 22-24    |
| 14. A Special Circuit, a Shift Register | 24-25    |
| 15. Counters                            | 25-26    |
| 16. Newer Computer Circuits             | 26-27    |
| 17. Conclusions                         | 27       |

## List of Illustrations and Tables

| Figure<br>Or Table # | Title  | Page # |
|----------------------|--|--------|
| Table 2.1            | Counting in Binary   | 4      |
| Table 2.2            | Counting in Octal, only 27 of 64 Possible Numbers are shown                  | 5      |
| Table 3.1            | Using 4 Bits to Count from 0 to 15 in Decimal or 0 to F in Hex               | 6      |
| Table 4.1            | The BCD Numbering System Derived from Binary                                 | 6      |
| Figure 5.1           | Representation of an AND Logic Circuit and Its Truth Table                   | 7      |
| Figure 5.2           | 3 Input AND gate and Truth Table   | 7      |
| Figure 5.3           | Minterm Maps for 2, 3, and 4 Input AND Gates                                 | 7      |
| Figure 5.4           | Sketch Showing How a Binary Bit Can Be Either a<br>Logic Element or a Number | 8      |
| Figure 5.5           | Picture of the Symbol, Truth Table, and Minterm Map<br>of a 2 Input OR Gate  | 8      |
| Figure 5.6           | Three Input OR Gate with Its Truth Table and Minterm Map                     | 9      |
| Figure 5.7           | Diagram of an NOT Gate and Its Truth Table                                   | 9      |

|                    |   |           |
|--------------------|---|-----------|
| <b>Figure 6.1</b>  | <b>Symbol, Truth Table and Minterm Map for a Two Input NAND Gate</b>                            | <b>9</b>  |
| <b>Figure 6.2</b>  | <b>Symbol, Truth Table, and Minterm Map for a Two Input NOR Gate</b>                            | <b>10</b> |
| <b>Table 7.1</b>   | <b>Table Showing What Happens When Two 1 Bit Binary Numbers Are Added</b>                       | <b>10</b> |
| <b>Figure 7.1</b>  | <b>XOR Circuit Made from AND's, OR's, and NOT's; and XOR Truth Table</b>                        | <b>10</b> |
| <b>Figure 8.1</b>  | <b>Two to One Multiplexor</b>   | <b>11</b> |
| <b>Figure 8.2</b>  | <b>Four to One Multiplexor</b>  | <b>12</b> |
| <b>Figure 8.3</b>  | <b>Multiplexor Circuit to Pick One of Four Inputs</b>   | <b>12</b> |
| <b>Figure 8.4</b>  | <b>Schematic Representations of a 1 to 2 and a 1 to 4 De Multiplexor</b>                        | <b>13</b> |
| <b>Figure 8.5</b>  | <b>A way to make a De Multiplexor</b>   | <b>13</b> |
| <b>Figure 9.1</b>  | <b>Some of the Rules of Boolean Algebra</b>   | <b>13</b> |
| <b>Figure 9.2</b>  | <b>Truth Table and Minterm Map for DeMorgan's Theorems</b>                                      | <b>14</b> |
| <b>Figure 9.3</b>  | <b>A Modification of DeMorgan's Theorem</b>   | <b>14</b> |
| <b>Figure 10.1</b> | <b>HALF ADDER Symbol, HALF ADDER Circuit, and HALF ADDER Truth Table</b>                        | <b>14</b> |
| <b>Figure 11.1</b> | <b>Symbol for a FULL ADDER and Its Truth Table</b>  | <b>15</b> |
| <b>Figure 11.2</b> | <b>One Way to Implement a FULL ADDER</b>  | <b>15</b> |
| <b>Figure 11.3</b> | <b>Classical Way to Implement a Full Adder with Two Half Adders and an OR</b>                   | <b>16</b> |
| <b>Figure 11.4</b> | <b>Truth Table for Figure 8.3</b>   | <b>16</b> |
| <b>Figure 12.1</b> | <b>Picture of Donut Shaped Magnetic Core Showing How It Can Be Magnetized in Two Directions</b> | <b>17</b> |
| <b>Figure 12.2</b> | <b>Magnetic Core Showing X and Y Current Pulse Wires and Sense Wire</b>                         | <b>17</b> |
| <b>Figure 12.3</b> | <b>Simple Transistor Flip Flop</b>  | <b>18</b> |
| <b>Figure 12.4</b> | <b>Symbol for a JK Flip Flop and Its Truth Table</b>  | <b>19</b> |
| <b>Figure 12.5</b> | <b>Symbol, Truth Table, and Timing for a T or Toggle Flip Flop</b>                              | <b>19</b> |
| <b>Figure 12.6</b> | <b>Symbol for and Truth Table of a Set Reset (SR) Flip Flop</b>                                 | <b>20</b> |
| <b>Figure 12.7</b> | <b>Symbol for and Truth Table of a D Flip Flop</b>  | <b>20</b> |
| <b>Figure 13.1</b> | <b>Square Wave Signal That Can Be Used As a Computer Timing Signal</b>                          | <b>22</b> |
| <b>Figure 13.2</b> | <b>NE555 Timer Used As a Square Wave Oscillator</b>   | <b>22</b> |
| <b>Figure 13.3</b> | <b>Schematic of a Pierce Crystal Controlled Oscillator</b>                                      | <b>23</b> |
| <b>Figure 14.1</b> | <b>Serial In Parallel Out Shift Register Showing Operation</b>                                  | <b>24</b> |
| <b>Figure 15.1</b> | <b>Presentation of an Eight Bit Binary Counter</b>  | <b>25</b> |
| <b>Figure 15.2</b> | <b>A Three Bit Ripple Counter</b>   | <b>25</b> |
| <b>Figure 15.3</b> | <b>Truth Table for a Toggle Flip Flop</b>   | <b>26</b> |
| <b>Figure 15.4</b> | <b>Timing Diagram Showing How a Counter Built from Toggle Flip Flops Work</b>                   | <b>26</b> |
| <b>Figure 15.5</b> | <b>Three Bit Synchronous Counter Built with Clocked Toggle Flip Flops</b>                       | <b>27</b> |
| <b>Figure 15.6</b> | <b>Timing Diagram and Counting Chart for the Counter of Figure 15.5</b>                         | <b>28</b> |
| <b>Figure 16.1</b> | <b>Chart of Number of Transistors Versus Date Showing Moore's Law</b>                           | <b>28</b> |

## 1. Introduction

The digital computer has had an amazing impact on our way of life. Starting with first computers in the early 1940's to the present time is less than one century. In this less than 100 year span, we have gone from electrical mechanical marvels and vacuum tubes to electronic solid state devices with very few moving parts that operate almost flawlessly. Where computer mean time between failures was measured in days or even hours, a standard desk top or lap top computer is expected to run for years with no time off for good behavior, or maybe I should call it bad behavior. My own desktop has run almost continuously for 8 years, with the only failure being one of the output devices, the screen. It was replaced by an out of the box, plug in replacement for less than \$200. It runs on 20% of the power of the one that burned out. So, to get on with the subject, some basic theory, let's proceed.

## 2. The Binary Number System

No series on digital computers would be complete without a review of the binary number system. The binary number system has only two digits, 1 and 0. This is very convenient because there are many electrical devices and circuits devices that only have two states. A switch can be on or off. We can let off be 0 and on be 1, or vice versa. A simple transistor circuit can be turned on or off. The on and off states can be thought of as a presence of some voltage (call this 1) and zero volts (call this 0).

The first thing that we need to do is to count in binary. Look at Table # 2.1.

| $2^2$ | $2^1$ | $2^0$ | Decimal |
|-------|-------|-------|---------|
| 0     | 0     | 0     | 0       |
| 0     | 0     | 1     | 1       |
| 0     | 1     | 0     | 2       |
| 0     | 1     | 1     | 3       |
| 1     | 0     | 0     | 4       |
| 1     | 0     | 1     | 5       |
| 1     | 1     | 0     | 6       |
| 1     | 1     | 1     | 7       |

**Table 2.1 Counting in Binary**

The decimal number is equal to the binary digit in the  $2^0$  place (0 or 1) times 1 (which is  $2^0$ ) plus the binary digit in the  $2^1$  place times 2 (which is  $2^1$ ) plus the binary digit in the  $2^2$  place times 4 (which is  $2^2$ ). The binary number needs more bits than three if we want to count higher than 7. Notice that counting to 7 is actually 8 positions, since 0 counts as part of the numbering sequence. As a matter of interest, we can take groups of 3 binary digits, as shown, and call it an octal numbering system. Table 1.2 shows this. The column on the left is counted as that digit times  $8^1$  (or 8). The column in the center is counted as that digit times  $8^0$  (or 1). Since showing all of the combinations would give a table counting to 77 octal (base 8), or 63 decimal (base 10) numbers, only 27 of 64 possible numbers are given. For fun, you might want to list all of the possible octal numbers from 00 to 77 and show their binary and decimal equivalents. One way to do this is to count from 000 000 to 111 111 in binary. Then list the octal and decimal equivalents.

| Octal          |                |         | Octal          |                |         | Octal          |                |         | Octal          |                |         |
|----------------|----------------|---------|----------------|----------------|---------|----------------|----------------|---------|----------------|----------------|---------|
| 8 <sup>1</sup> | 8 <sup>0</sup> | Decimal | 8 <sup>1</sup> | 8 <sup>0</sup> | Decimal | 8 <sup>1</sup> | 8 <sup>0</sup> | Decimal | 8 <sup>1</sup> | 8 <sup>0</sup> | Decimal |
| 0              | 0              | 0       | 1              | 0              | 8       | 0              | 0              | 0       | 0              | 0              | 0       |
| 0              | 1              | 1       | 1              | 1              | 9       | 1              | 0              | 8       | 1              | 1              | 9       |
| 0              | 2              | 2       | 1              | 2              | 10      | 2              | 0              | 16      | 2              | 2              | 18      |
| 0              | 3              | 3       | 1              | 3              | 11      | 3              | 0              | 24      | 3              | 3              | 27      |
| 0              | 4              | 4       | 1              | 4              | 12      | 4              | 0              | 32      | 4              | 4              | 36      |
| 0              | 5              | 5       | 1              | 5              | 13      | 5              | 0              | 40      | 5              | 5              | 45      |
| 0              | 6              | 6       | 1              | 6              | 14      | 6              | 0              | 48      | 6              | 6              | 54      |
| 0              | 7              | 7       | 1              | 7              | 15      | 7              | 0              | 56      | 7              | 7              | 63      |

*To view the remainder of the course material and to take the quiz for PDH credit, you must purchase the course.*

*Close this window and click "Add to cart" on the product page.*

There are  
of 3 binary  
use 33<sub>8</sub>, w  
When work  
simplify wh  
is still used  
keep track o  
system is cal

### 3. The F

Whereas the c  
and has 16 po  
memory organ  
binary because  
hexadecimal is  
For example, a  
hexadecimal or  
the number of c  
are usually give  
still 1111.

Table 3.1 shows  
Hexadecimal num  
is used, imagine the 32 bit digital number (0101 0001 1101 0111). Looking at that string of 0's and 1's can easily confuse most people. If we broke that 32 bit number into 4 groups of 4 bits each, and used Hexadecimal notation, this could be read as (51D7). Check this out by referring to Chart 3.1. Admittedly, this is still a bit cryptic, but it is definitely easier to read than 0101000111010111. The reason for learning to think in terms of binary, octal, and hexadecimal is that most modern computers are based on a binary system. IBM compatible machines have a memory that is based on 8 bit bytes. If we want to look at what is in those 8 bit bytes, a single character, 0 to F is easier than a 4 bit string of 0's and 1's. We will now look at a special form of 4 bit groups called Binary Coded Decimal.

vn  
pens is that groups  
(check this out), we  
33<sub>8</sub> than 011011<sub>2</sub>.  
ven a code name to  
tem of numbering  
hat it is easier to  
numbering

tem uses 4 bits  
byte system of  
tal instead of  
r of fact  
hexadecimal.  
3  
15. To keep  
rs 10 to 15  
f 15 (F) is